

Assignment 3

16-bit ALU

Introduction: -

ALU is the fundamental building block of the processor, which is responsible for carrying out the **unsigned arithmetic**, **logic** functions, **Shift** functions and **Comparison** functions.

Specification:

- **ALU Operands** (A, B)
- **ALU Result** (ALU_OUT)
- ALU operands and output Result are of **16-bit** width.
- **ALU Result (ALU_OUT) is registered.**
- The ALU function is carried out according to the value of the **ALU_FUN** input signal stated in the table in the following page and any other value for **ALU_FUN** not stated in the table, **ALU_OUT** must equal to **16'b0**
- **Carry_Flag** represents the carry bit in case of addition and the borrow in case of subtraction.
- **Arith_flag** is activated "High" only when ALU performs one of the arithmetic operations (Addition, Subtraction, Multiplication, division), otherwise "LOW"
- **Logic_flag** is activated "High" only when ALU performs one of the Boolean operations (AND, OR, NAND, NOR, XOR, XNOR), otherwise "LOW"
- **CMP_flag** is activated "High" only when ALU performs one of the Comparison operations (Equal, Greater than, less than), otherwise "LOW"
- **Shift_flag** is activated "High" only when ALU performs one of the shifting operations (shift right, shift left), otherwise "LOW"


ALU_FUN Table

ALU_FUN	Operation	ALU_OUT
0000	Arithmetic : unsigned Addition	
0001	Arithmetic : unsigned Subtraction	
0010	Arithmetic : unsigned Multiplication	
0011	Arithmetic : unsigned Division	
0100	Logic : AND	
0101	Logic : OR	
0110	Logic : NAND	
0111	Logic : NOR	
1000	Logic : XOR	
1001	Logic : XNOR	
1010	CMP: A = B	Equal to 1 else Equal to 0
1011	CMP: A > B	Equal to 2 else Equal to 0
1100	CMP: A < B	Equal to 3 else Equal to 0
1101	SHIFT: A >> 1	
1110	SHIFT: A << 1	

Hint: Use Case statement to describe the behavior of this table and use default case if needed.

Hint: You can use if statement inside case branches

Block Interface

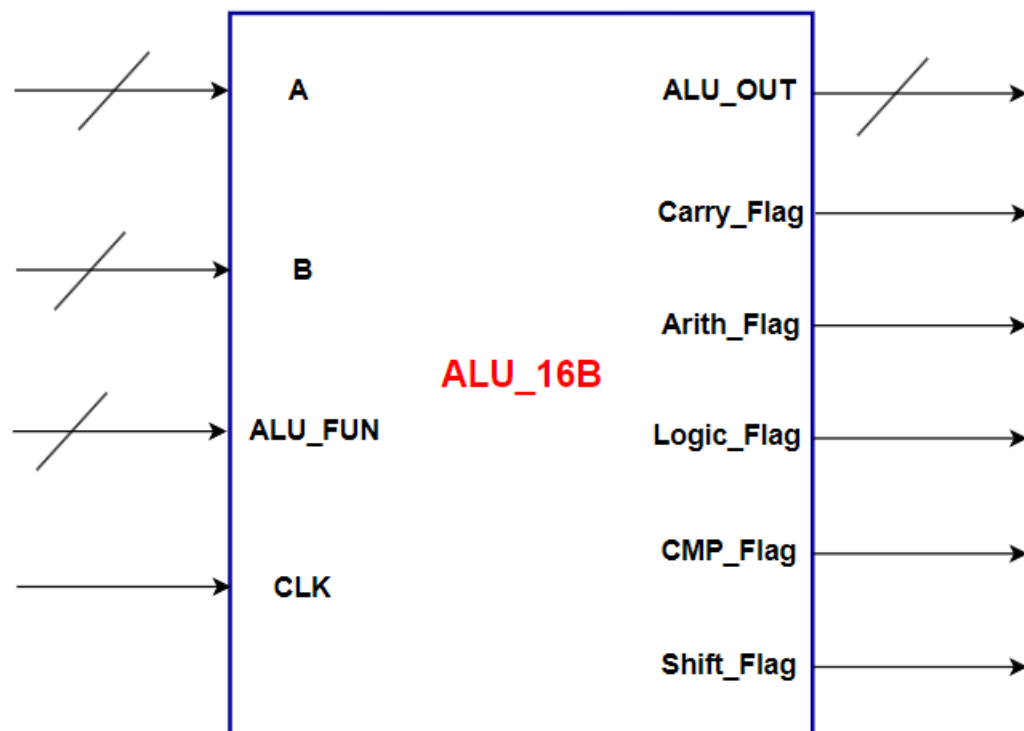

Requirements

1. Write a Verilog Code to capture the above specifications
2. Write a testbench to test all the ALU functions to include **at least** the following **16 test cases**: -
 - Unsigned Arithmetic Operations (Addition, Subtraction, Multiplication, Division)
 - Logical Operations (AND, NAND, OR, NOR)
 - Compare Operations (Equal, Greater, Less)
 - Shift Operations (A shift right, A shift left, B shift right, B shift left)
 - NOP
3. Write a testbench to test all the ALU functions with operating clock frequency **100 KHz**
4. Synthesis Diagram of your code using **draw.io** online tool